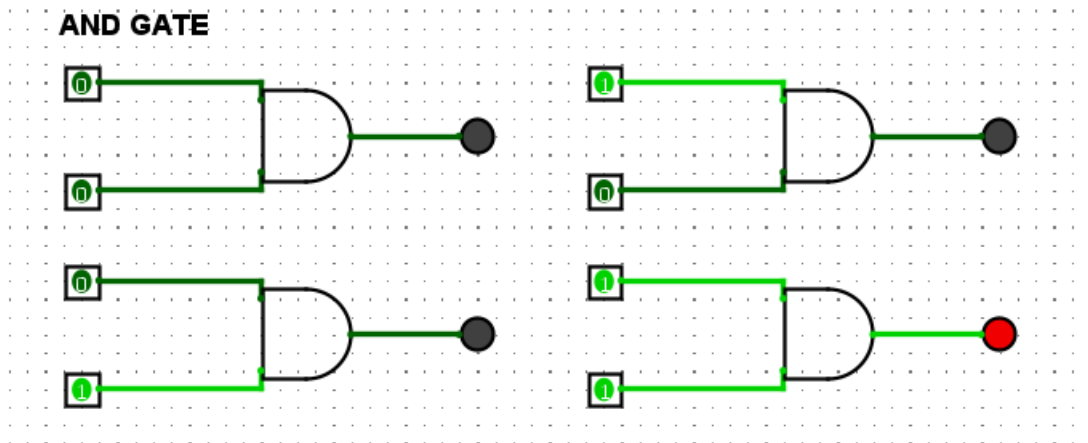



AND GATE truth table:

Pin 1	Pin 2	Output
0	0	OFF
0	1	OFF
1	0	OFF
1	1	ON




NOT GATE truth table:

Pin	Output
0	ON
1	OFF

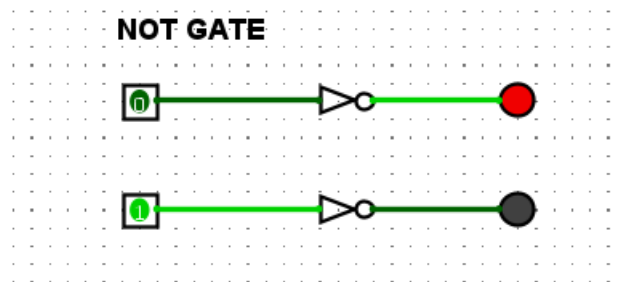


XOR GATE truth table:

Pin 1	Pin 2	Output
0	0	OFF
0	1	ON
1	0	ON
1	1	OFF

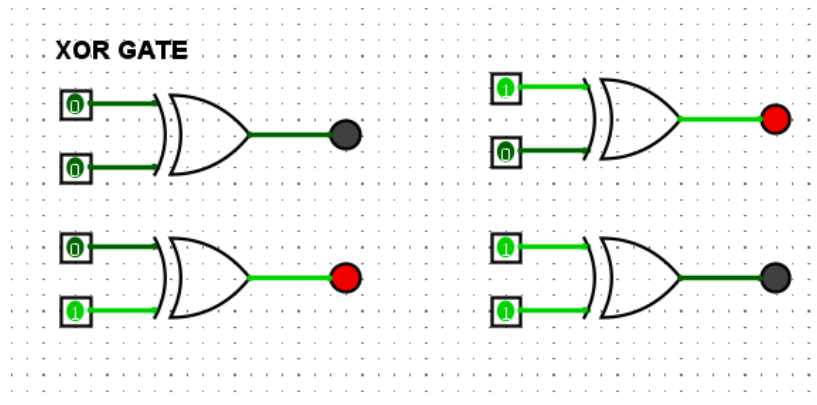

Question 12

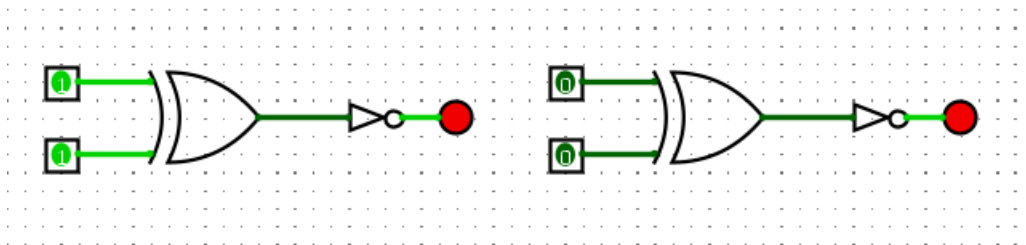

Question 15 (3 way input

